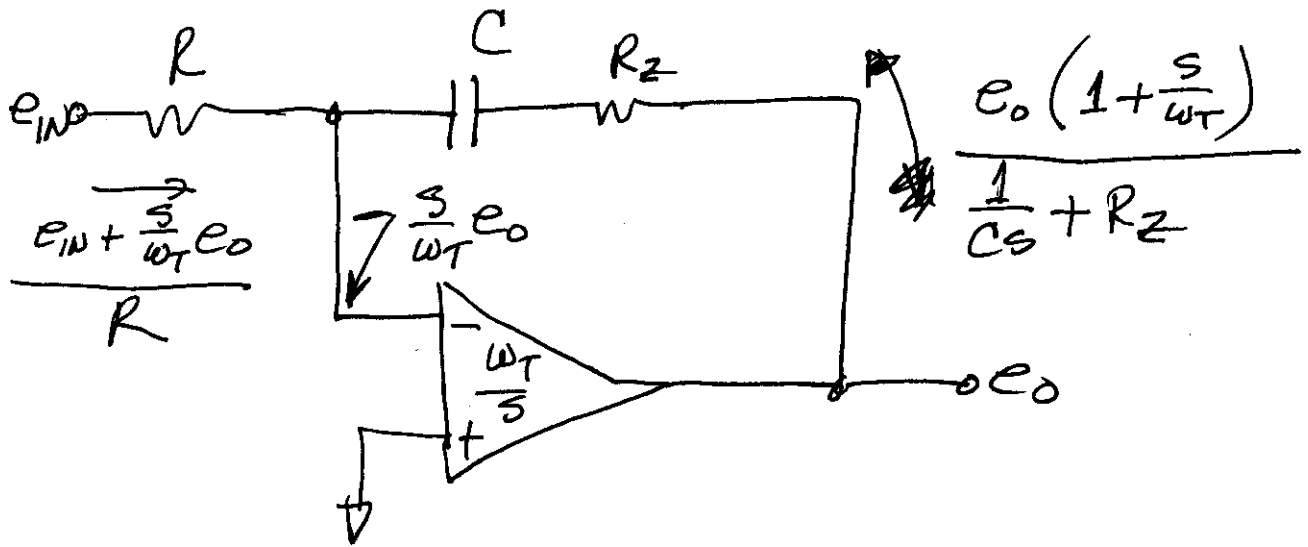


SIMPLISTICALLY



$$\frac{e_{IN} + \frac{s}{\omega_T} e_O}{R} = \frac{e_O \left(1 + \frac{s}{\omega_T}\right)}{\frac{1}{Cs} + R_2} = \frac{Cs e_O \left(1 + \frac{s}{\omega_T}\right)}{R_2 Cs + 1}$$

$$\frac{e_{IN} + \frac{s}{\omega_T} e_O}{R} = \frac{Cs e_O \left(1 + \frac{s}{\omega_T}\right)}{R_2 Cs + 1}$$

$$e_{IN} + \frac{s}{\omega_T} e_O = \frac{RCs e_O \left(1 + \frac{s}{\omega_T}\right)}{R_2 Cs + 1}$$

$$\text{SET } R_2 C = \frac{1}{\omega_T}$$

$$e_{IN} + \frac{s}{\omega_T} e_O = RCs e_O$$

$$e_{IN} = e_O \left(RCs - \frac{s}{\omega_T} \right) = s e_O \left(RC - \frac{1}{\omega_T} \right)$$

$$e_O = \frac{1}{s} e_{IN} \frac{1}{RC - \frac{1}{\omega_T}} \equiv \text{PERFECT INTEGRATOR WITH GAIN ERROR: } \frac{\omega_T}{\omega_T RC - 1}$$