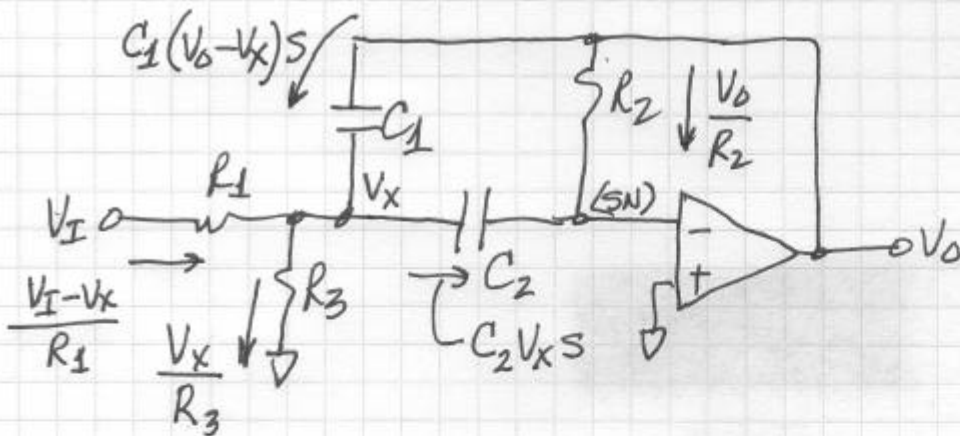


# Ugly Xfer Function

①



AT NODE SN:  $C_2 V_x s + \frac{V_o}{R_2} = 0$

THUS:  $V_x = -\frac{V_o}{R_2 C_2 s}$

AT NODE  $V_x$ :  $\frac{V_I - V_x}{R_1} - \frac{V_x}{R_3} + C_1 (V_o - V_x) s - C_2 V_x s = 0$

COLLECTING TERMS:

$$\frac{V_I}{R_1} + C_1 V_o s = V_x \left[ \frac{1}{R_1} + \frac{1}{R_3} + C_1 s + C_2 s \right]$$

THEN:  $V_x = \frac{\frac{V_I}{R_1} + C_1 V_o s}{\frac{1}{R_1} + \frac{1}{R_3} + (C_1 + C_2) s} = -\frac{V_o}{R_2 C_2 s}$

$$\frac{V_I}{1 + \frac{R_1}{R_3} + R_1 (C_1 + C_2) s} = -V_o \left[ \frac{1}{R_2 C_2 s} + \frac{C_1 s}{\frac{1}{R_1} + \frac{1}{R_3} + (C_1 + C_2) s} \right]$$

$$\frac{V_I}{1 + \frac{R_1}{R_3} + R_1 (C_1 + C_2) s} = -V_o \left[ \frac{1}{R_2 C_2 s} + \frac{R_1 C_1 s}{1 + \frac{R_1}{R_3} + R_1 (C_1 + C_2) s} \right]$$

$$\frac{V_1}{1 + \frac{R_1}{R_3} + R_1(C_1 + C_2)s} = -V_0 \left[ \frac{1 + \frac{R_1}{R_3} + R_1(C_1 + C_2)s + R_2 C_2 R_1 C_1 s^2}{\{R_2 C_2 s\} * \{1 + \frac{R_1}{R_3} + R_1(C_1 + C_2)s\}} \right] \quad (2)$$

$$V_0 = -V_1 \frac{R_2 C_2 s}{R_1 R_2 C_1 C_2 s^2 + R_1(C_1 + C_2)s + 1 + \frac{R_1}{R_3}}$$


$$\text{GAIN} = \frac{R_2 C_2}{R_1(C_1 + C_2)}$$

$$f_{\text{CENTER}} = \frac{1}{2\pi} \sqrt{\frac{(1 + R_1/R_3)}{R_1 R_2 C_1 C_2}}$$

$$\text{Bandwidth} = \frac{1}{2\pi} \cdot \frac{(C_1 + C_2)}{R_2 C_1 C_2}$$

# Gyrator BP Filter

(3)

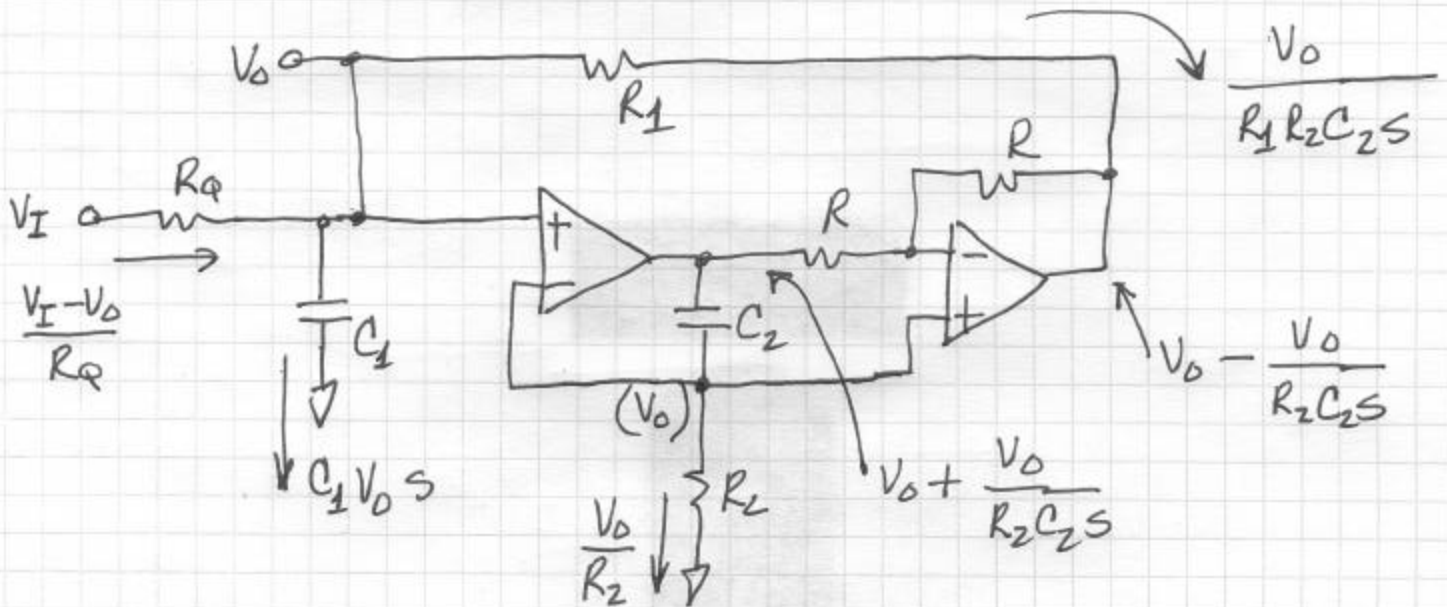

SUM CURRENTS AT  $V_O$  NODE:

$$\frac{V_I - V_O}{R_Q} - C_1 V_O S - \frac{V_O}{R_1 R_2 C_2 S} = 0$$

$$\frac{V_I}{R_Q} = V_O \left[ \frac{1}{R_Q} + C_1 S + \frac{1}{R_1 R_2 C_2 S} \right]$$

$$V_I = V_O \left[ 1 + R_Q C_1 S + \frac{R_Q}{R_1 R_2 C_2 S} \right]$$

$$V_O = V_I * \frac{R_1 R_2 C_2 S}{R_Q R_1 R_2 C_1 C_2 S^2 + R_1 R_2 C_2 S + R_Q}$$

$$V_O = V_I * \frac{\frac{R_1 R_2 C_2 S}{R_Q}}{R_1 R_2 C_1 C_2 S^2 + \frac{R_1 R_2 C_2 S}{R_Q} + 1}$$

GAIN = 1       $f_{\text{CENTER}} = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$       BANDWIDTH =  $\frac{1}{2\pi R_Q C_1}$

↑ INDEPENDENT ↓